

+40

2

Problem One: Consider the circuit shown below. (40 points)

The source voltage $v_s(t) = 100 \sin(5000t + 30^\circ) \text{ V}$, find the following:


- 1- The current $i(t)$.
- 2- The voltage, $v_c(t)$, across the capacitor.
- 3- Draw the Phasor diagram to show the phasors of the current I and the capacitor voltage V_c .

$$\omega = 5000$$

$$V_s = 100 \sin(5000t + 30^\circ)$$

$$= 100 \cos(5000t - 60^\circ)$$

$$= 100 \angle -60^\circ \text{ V}$$

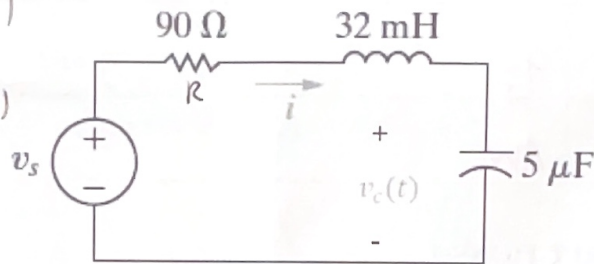

$$X_L = j\omega L = j(32 \cdot 10^{-3})(5000) = j160 \Omega$$

$$X_C = \frac{-j}{\omega C} = \frac{-j}{5000 \cdot (5 \cdot 10^{-6})} = -j40 \Omega$$

$$Z_{\text{Total}} = R + X_L + X_C = 90 \Omega + j120 \Omega = j120$$

$$\therefore Z_{\text{Total}} = 150 \angle 53.13^\circ \Omega$$



1. From Ohm's Law:

$$I = \frac{V}{R} \rightarrow i(t) = \frac{V_s}{Z_{\text{Total}}} = \frac{100 \angle -60^\circ}{150 \angle 53.13^\circ}$$

$$i(t) = \frac{2}{3} \angle -113.13^\circ = \frac{2}{3} \cos(5000t - 113.13^\circ) \text{ A}$$

This page is left blank for your work.

2. In a series circuit, current is the same for all elements.


By Ohm's law: $V = IR \rightarrow V_L(t) = i(t) \cdot X_L$

$$= \frac{2}{3} \underline{1.13.13} \cdot \overset{2 \quad 40 \angle -90}{\underline{-j40}} \quad V_L(t) = \underline{\underline{\frac{80}{3} \angle -203.13^\circ \text{ V}}}$$

$$= \frac{80}{3} \cos(5000t - 203.13^\circ)$$

3.


Phasor diagram:

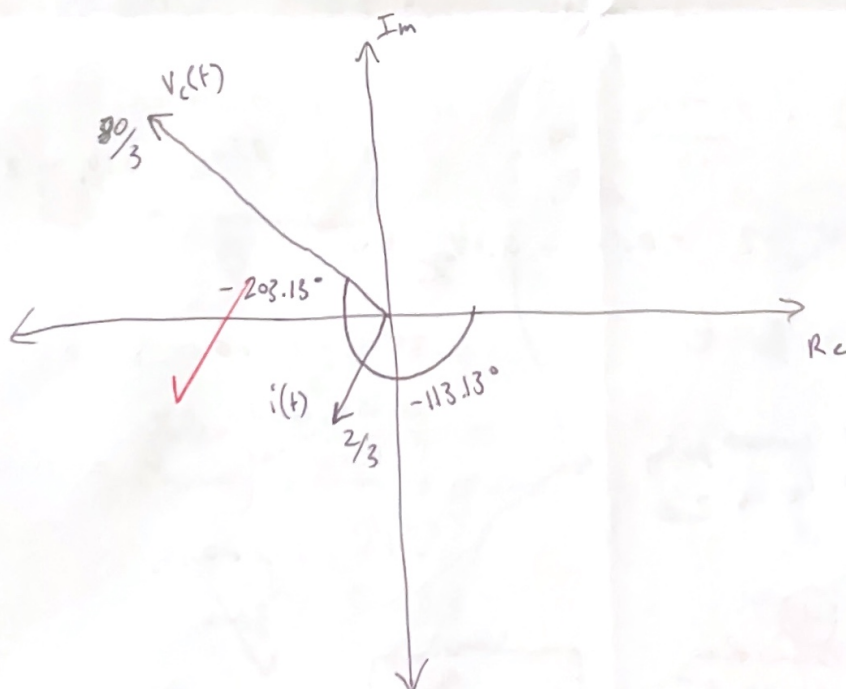

+19

4

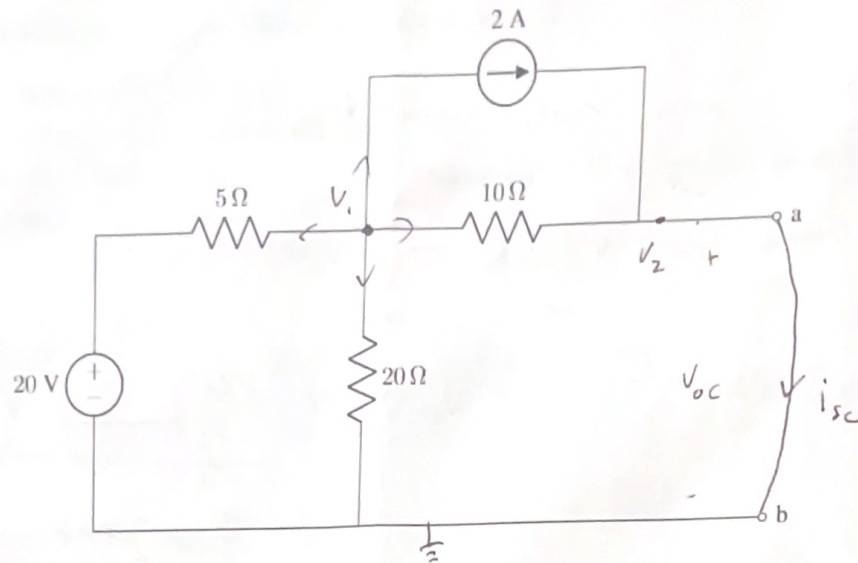Problem Two: Consider the circuit shown below. (25 points)



Obtain the Thevenin equivalent circuit across terminals a-b of the circuit shown.

[2] node voltage analysis @ node V_1 !

@ V_2 !

$$\frac{V_1 - 20}{5} + \frac{V_1}{20} + 2 + \frac{V_1 - V_2}{10} = 0$$

$$\frac{V_2 - V_1}{10} = 2$$

$$0.1V_2 - 0.1V_1 = 2 \quad (2)$$

$$0.2V_1 - 4 + 0.05V_1 + 2 + 0.1V_1 - 0.1V_2 = 0$$

$$0.35V_1 - 0.1V_2 = 2 \quad (1)$$

$$0.35V_1 - (2 + 0.1V_1) = 2$$

$$0.35V_1 - 0.1V_1 = 4$$

$$0.25V_1 = 4 \quad V_1 = 16V$$

$$0.1V_2 = 2 + 0.1V_1$$

$$= 36V$$


$$V_{oc} = V_2$$

∴ only current going to I_x is 2A

$$\rightarrow V_{oc} = 36V$$

$$I_{sc} = 2A$$


$$R_{th} = 2\Omega$$

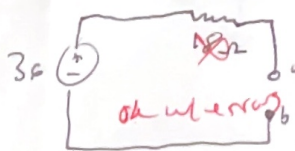

+20


5

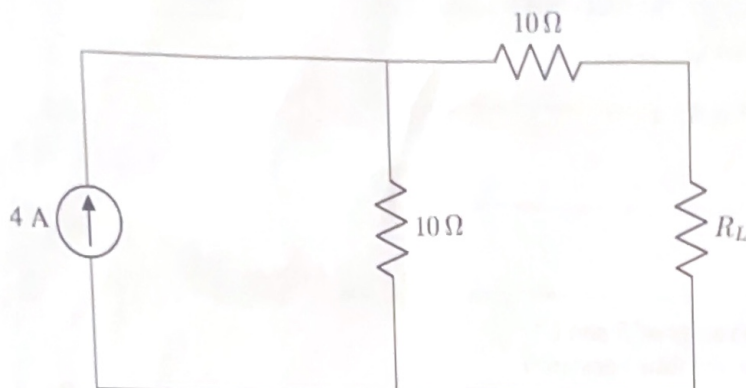Problem Three: Consider the circuit shown below: (20 points)



- 1- Find R_L for maximum power deliverable to R_L
- 2- Determine that maximum power.

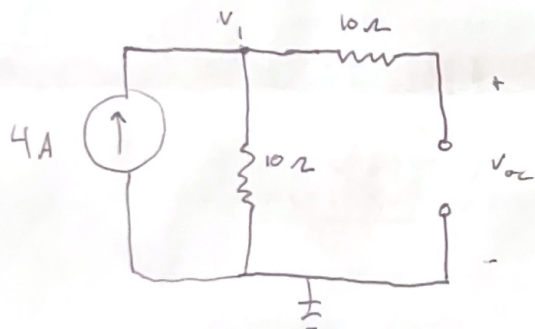To find R_L , need R_{th} : redraw circuit w/ open circuit in place of R_L .



note voltage analysis @ V_1 :

$$\frac{V_1 - V_{oc}}{10} + \frac{V_1}{10} = 4$$

$$\text{@ } V_{oc}: \frac{V_{oc} - V_1}{10} = 0$$

$$0.1V_{oc} = 0.1V_1$$

$$V_1 = V_{oc}$$

$$\frac{V_1}{10} = 4$$

$$V_1 = 40V$$

$$V_{oc} = 40V$$

Current source splits evenly between 2 10Ω resistors!

$$I_{sc} = 2A$$

$$R_{th} = 20\Omega$$

$$R_L = 20\Omega$$

5 | Page

$$P_{Lmax} = \frac{(V_{oc})^2}{4R_L} = 20W$$

for max power, $R_L = R_{th}$

+12


6

Problem Four: Consider the circuit shown below. (15 points)

In the circuit shown, the following is observed.

$$v(t) = 56e^{-200t} \text{ V, } t > 0$$

$$i(t) = 8e^{-200t} \text{ mA, } t > 0$$

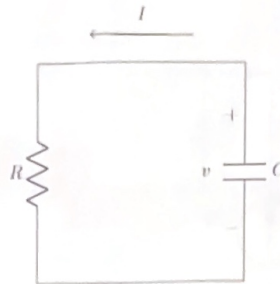

- 1- Find the values of R and C
- 2- Calculate the time constant τ
- 3- Determine the time required for the voltage to decay half its initial value at $t = 0$.

$$1. R = \frac{V}{I} = \frac{56e^{-200t}}{8e^{-200t}} = 7 \text{ k}\Omega \quad \text{①}$$

$$i(t) = C \frac{dv}{dt} \rightarrow C = \frac{dv}{dt} \cdot \frac{1}{i(t)} \quad \text{②}$$

$$C = \frac{d}{dt} [v(t)] = \frac{d}{dt} [56e^{-200t}] = -11200e^{-200t} \cdot \frac{1}{8e^{-200t}}$$

$$C = 1400 \text{ F}$$

$$2. \tau = RC = 7 \cdot 1400 = 9800$$

$$3. \text{ at } t=0, V = 56 \text{ V} \quad \text{OK}$$

$$\rightarrow 28 = 56e^{-200t}$$

$$0.5 = e^{-200t}$$

$$\ln(0.5) = -200t \rightarrow \frac{\ln(0.5)}{-200} = t = 0.00347 \text{ s}$$